

ECGR 4146: Introduction to VHDL

Lab 4: 2-Bit Comparator

Note: (I had an issue trying to run the design sources within the same project, so I created three separate project folders. For some reason, it would not work well if I tried to change the architecture name to something other than Behavioral)

VHDL Code for Dataflow Model:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity comparator2bitDataflow is
    Port ( a : in STD_LOGIC_VECTOR(1 downto 0);
          b : in STD_LOGIC_VECTOR(1 downto 0);
          eq : out STD_LOGIC);
end comparator2bitDataflow;
architecture Behavioral of comparator2bitDataflow is
    signal s0, s1, s2, s3: std_logic;
begin
    s0 <= (not a(1)) and (not a(0)) and (not b(1)) and (not b(0));
    s1 <= (not a(1)) and a(0) and (not b(1)) and b(0);
    s2 <= a(1) and (not a(0)) and b(1) and (not b(0));
    s3 <= a(1) and a(0) and b(1) and b(0);
    eq <= s0 or s1 or s2 or s3;
end Behavioral;
```

VHDL Testbench Code for Dataflow Model:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity comparator2bitDataflowsim is
    -- Port( );
end comparator2bitDataflowsim;
architecture Behavioral of comparator2bitDataflowsim is
    signal a : std_logic_vector(1 downto 0);
    signal b : std_logic_vector(1 downto 0);
    signal eq : std_logic;
begin
    p0:entity work.comparator2bitDataflow(Behavioral) port map(a=>a,b=>b,eq=>eq);
    process
    begin
        A <= "00";
        B <= "00";
        wait for 20ns;
        A <= "00";
        B <= "01";
        wait for 20ns;
        A <= "00";
        B <= "10";
        wait for 20ns;
```


```
A <= "00";
B <= "11";
wait for 20ns;

A <= "01";
B <= "00";
wait for 20ns;
A <= "01";
B <= "01";
wait for 20ns;
A <= "01";
B <= "10";
wait for 20ns;
A <= "01";
B <= "11";
wait for 20ns;

A <= "10";
B <= "00";
wait for 20ns;
A <= "10";
B <= "01";
wait for 20ns;
A <= "10";
B <= "10";
wait for 20ns;
A <= "10";
B <= "11";
wait for 20ns;

A <= "11";
B <= "00";
wait for 20ns;
A <= "11";
B <= "01";
wait for 20ns;
A <= "11";
B <= "10";
wait for 20ns;
A <= "11";
B <= "11";
wait for 20ns;
end process;
end Behavioral;
```

Simulation Waveform of Dataflow Model

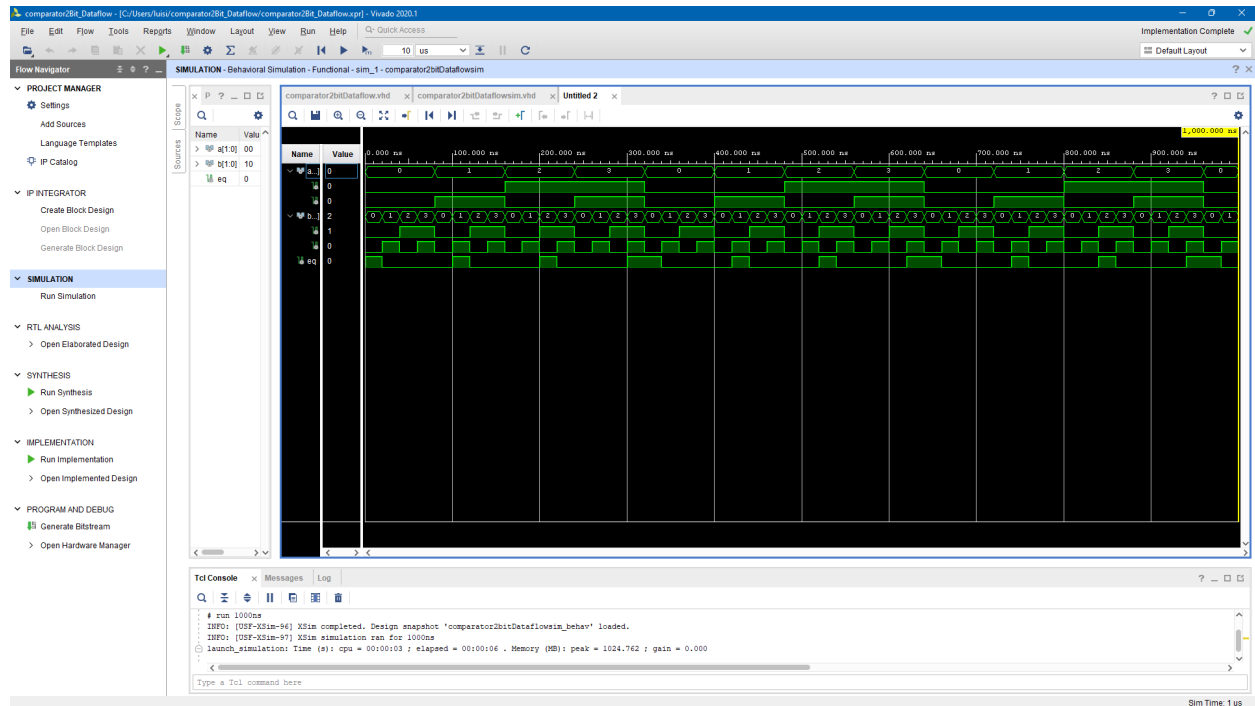

VHDL Code for Behavioral Model:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity comparator2bitBehaviorial is
    Port ( a : in STD_LOGIC_VECTOR(1 downto 0);
          b : in STD_LOGIC_VECTOR(1 downto 0);
          eq : out STD_LOGIC);
end comparator2bitBehaviorial;
architecture Behavioral of comparator2bitBehaviorial is
begin
process(a,b)
begin
    if (a(0)=b(0)) and (a(1)=b(1)) then
        eq <= '1';
    else
        eq<='0';
    end if;
end process;
end Behavioral;
```

VHDL Testbench Code for Behavioral Model:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity comparator2bitBehaviorialsim is
```

```
-- Port ( );
end comparator2bitBehavioralsim;
architecture Behavioral of comparator2bitBehavioralsim is
    signal a : std_logic_vector(1 downto 0);
    signal b : std_logic_vector(1 downto 0);
    signal eq : std_logic;
begin
    p0:entity work.comparator2bitBehaviorial(Behavioral) port map(a=>a,b=>b,eq=>eq);
    process
    begin
        A <= "00";
        B <= "00";
        wait for 20ns;
        A <= "00";
        B <= "01";
        wait for 20ns;
        A <= "00";
        B <= "10";
        wait for 20ns;
        A <= "00";
        B <= "11";
        wait for 20ns;


        A <= "01";
        B <= "00";
        wait for 20ns;
        A <= "01";
        B <= "01";
        wait for 20ns;
        A <= "01";
        B <= "10";
        wait for 20ns;
        A <= "01";
        B <= "11";
        wait for 20ns;

        A <= "10";
        B <= "00";
        wait for 20ns;
        A <= "10";
        B <= "01";
        wait for 20ns;
        A <= "10";
        B <= "10";
        wait for 20ns;
        A <= "10";
        B <= "11";
        wait for 20ns;

        A <= "11";
        B <= "00";
        wait for 20ns;
        A <= "11";
        B <= "01";
        wait for 20ns;
        A <= "11";
        B <= "10";
        wait for 20ns;
    end process
end;
```

```
A <= "11";  
B <= "11";  
wait for 20ns;  
end process;  
end Behavioral;
```

Simulation Waveform of Behavioral Model

 

VHDL Code for Structural Model

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
entity comparator2BitStructural is  
    Port ( a : in STD_LOGIC_VECTOR(1 downto 0);  
          b : in STD_LOGIC_VECTOR(1 downto 0);  
          eq : out STD_LOGIC);  
end comparator2BitStructural;  
architecture Behavioral of comparator2BitStructural is  
    signal s0, s1: std_logic;  
begin  
    eq_bit0: entity work.comparator1Bit  
        port map (a=>a(0), b=>b(0), eq=>s0);  
    eq_bit1: entity work.comparator1Bit  
        port map (a=>a(1), b=>b(1), eq=>s1);  
    eq <= s0 and s1;  
end Behavioral;
```

VHDL Testbench Code for Structural Model

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity comparator2BitStructuralsim is
-- Port ( );
end comparator2BitStructuralsim;
architecture Behavioral of comparator2BitStructuralsim is
signal a : std_logic_vector(1 downto 0);
  signal b : std_logic_vector(1 downto 0);
  signal eq : std_logic;
begin
p0:entity work.comparator2bitStructural(Behavioral) port map(a=>a,b=>b,eq=>eq);
process
begin
  A <= "00";
  B <= "00";
  wait for 20ns;
  A <= "00";
  B <= "01";
  wait for 20ns;
  A <= "00";
  B <= "10";
  wait for 20ns;
  A <= "00";
  B <= "11";
  wait for 20ns;

  A <= "01";
  B <= "00";
  wait for 20ns;
  A <= "01";
  B <= "01";
  wait for 20ns;
  A <= "01";
  B <= "10";
  wait for 20ns;
  A <= "01";
  B <= "11";
  wait for 20ns;

  A <= "10";
  B <= "00";
  wait for 20ns;
  A <= "10";
  B <= "01";
  wait for 20ns;
  A <= "10";
  B <= "10";
  wait for 20ns;
  A <= "10";
  B <= "11";
  wait for 20ns;

  A <= "11";
  B <= "00";
  wait for 20ns;
  A <= "11";
```

```
B <= "01";  
wait for 20ns;  
A <= "11";  
B <= "10";  
wait for 20ns;  
A <= "11";  
B <= "11";  
wait for 20ns;  
end process;  
end Behavioral;
```

Simulation Waveform of Structural Model

